



## Chapter 3

# Memory

These slides support chapter 3 of the book

*The Elements of Computing Systems*

By Noam Nisan and Shimon Schocken

MIT Press

# Chapter 3: Memory

---

## Time matters

- Sequential logic
- Flip Flops
- Memory units
- Counters
- Project 3 overview

# Time-independent logic

---

- So far we ignored the issue of *time*
- The chip's inputs were just “sitting there” – fixed and unchanging
- The chip's output was a pure function of the current inputs, and did not depend on anything that happened previously
- The output was computed “instantaneously”
- This style of gate logic is sometimes called:
  - *time-independent logic*
  - *combinational logic*.

# Hello, time

---

## Abstraction issues:

- The hardware must support maintaining “state”
- The hardware must support computations over time

example:


```
x = 17
```

example:


```
for i = 0 ... 99:  
    sum = sum + a[i]
```
 
## Implementation issues:


- The hardware must handle the *physical time delays* associated with calculating and moving data from one chip to another.




# Physical time / clock time

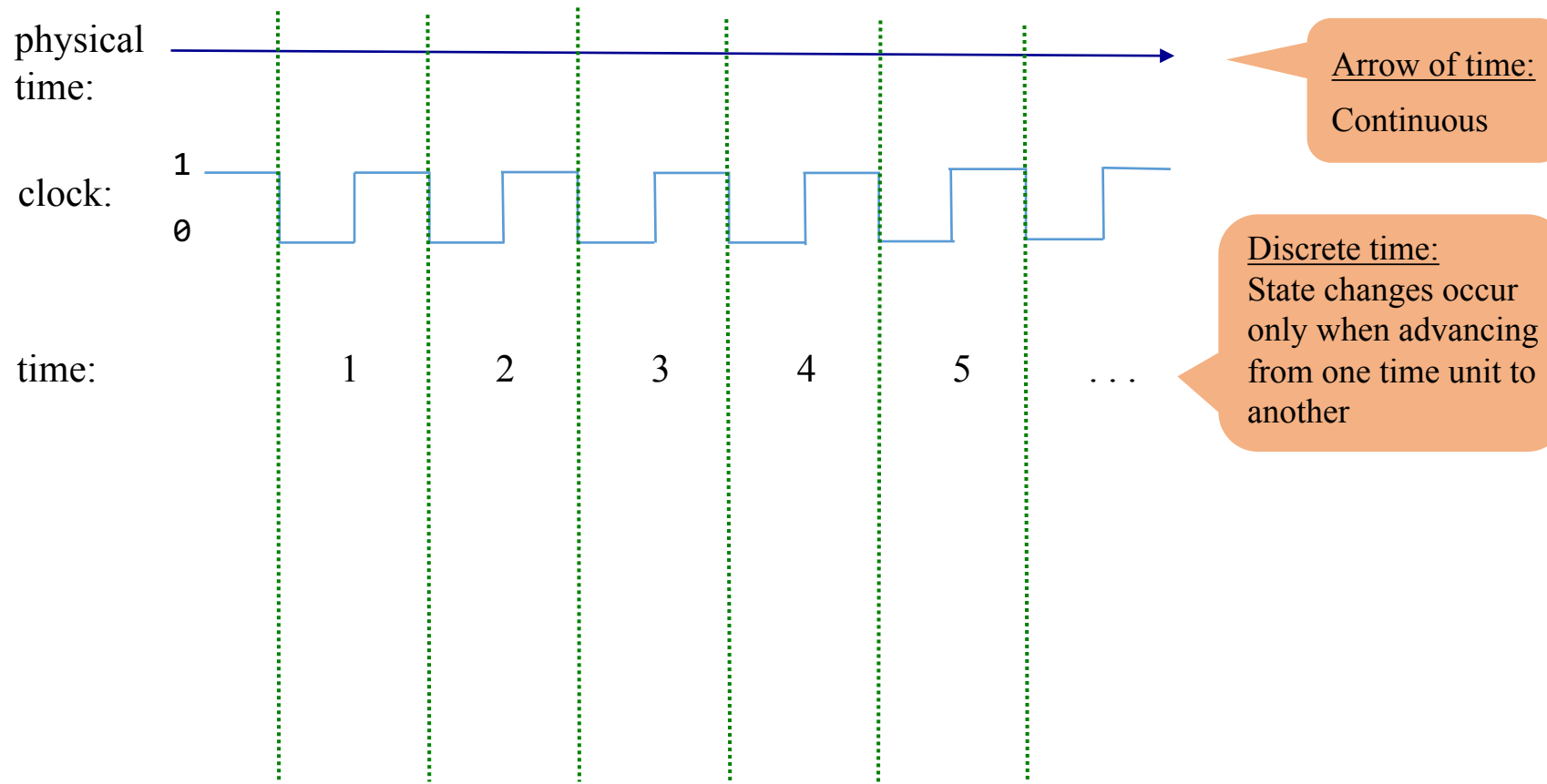


# Chip behavior over time (example)

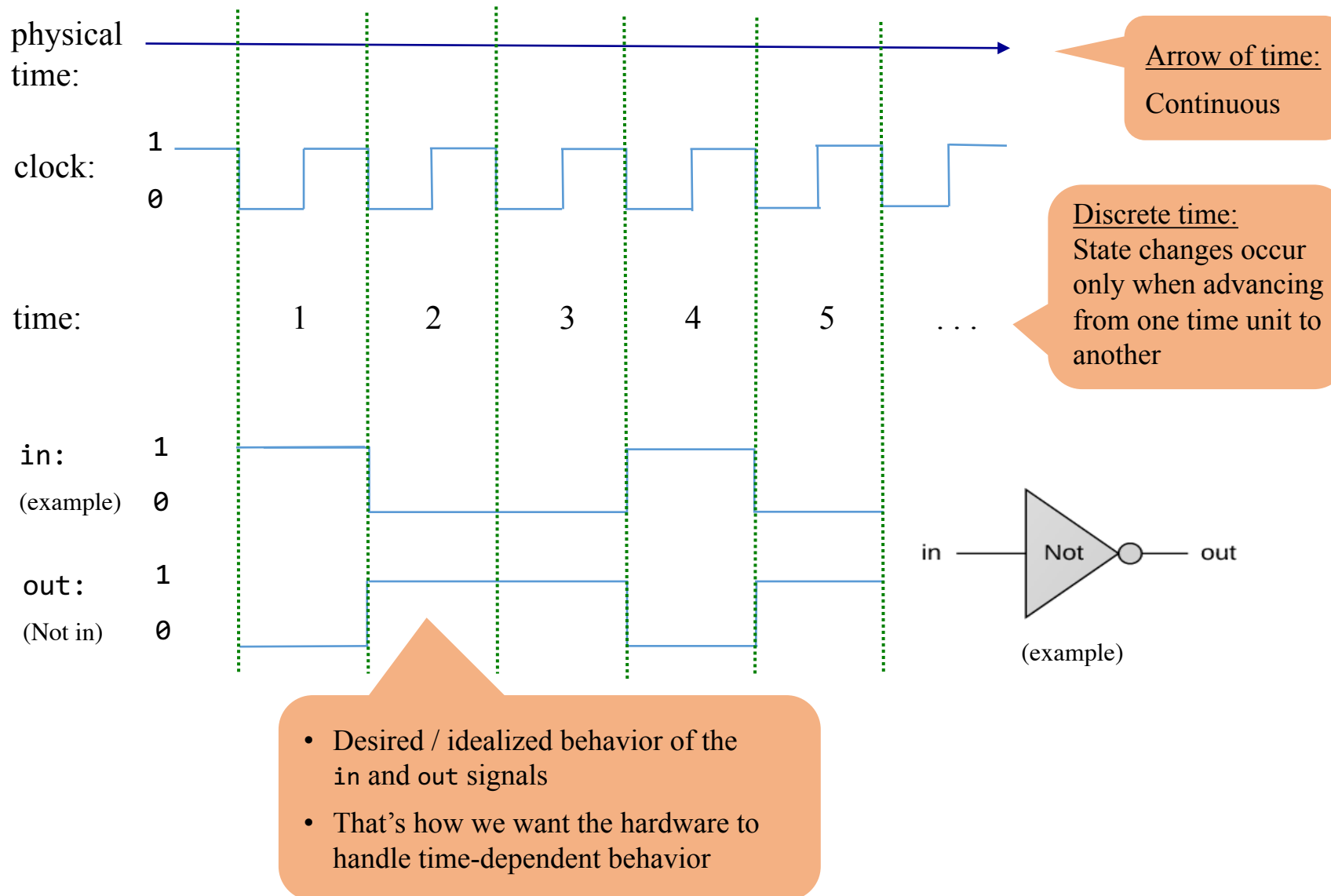

# Chip behavior over time (example)

 


# Chip behavior over time (example)

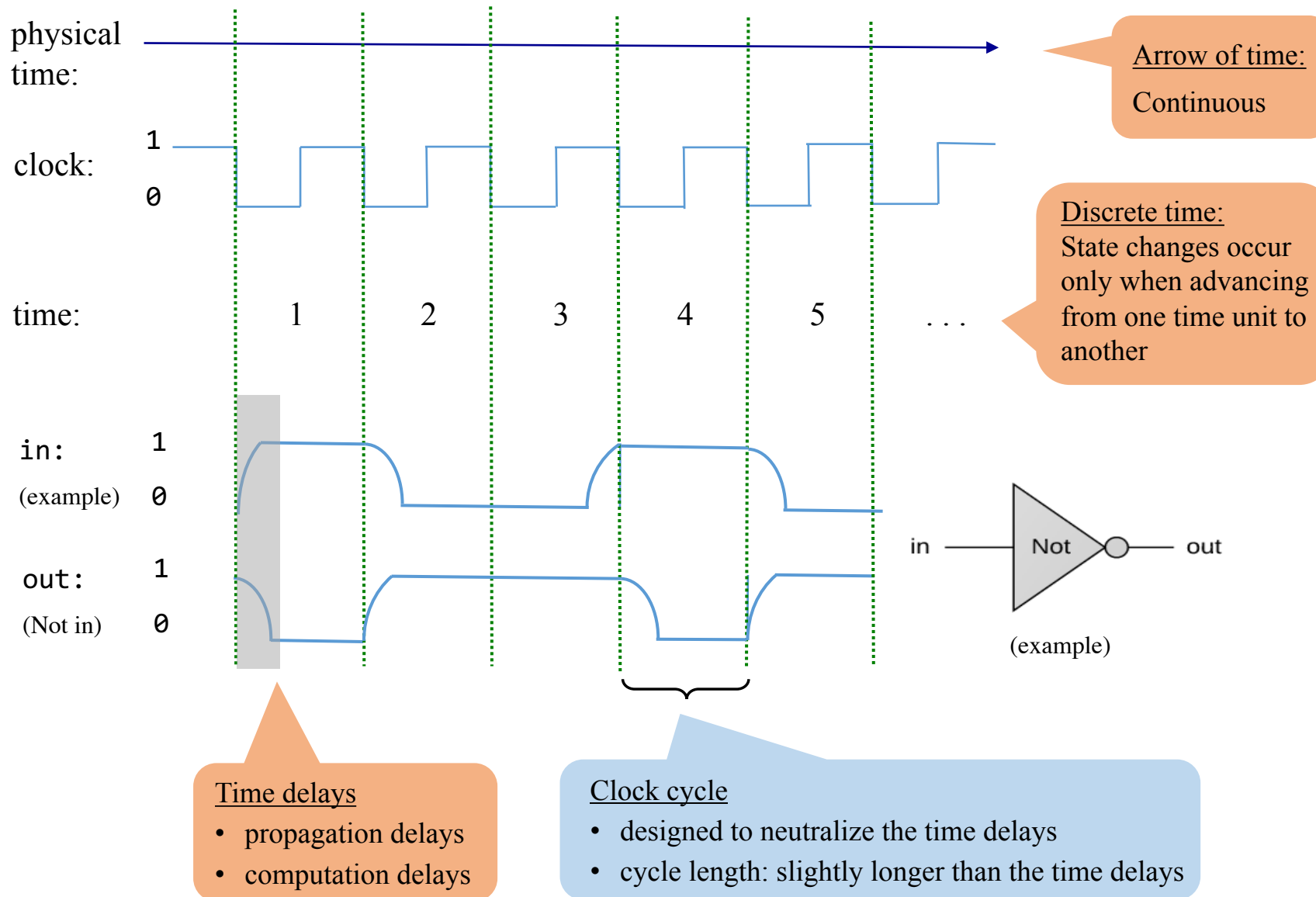



# Chip behavior over time (example)

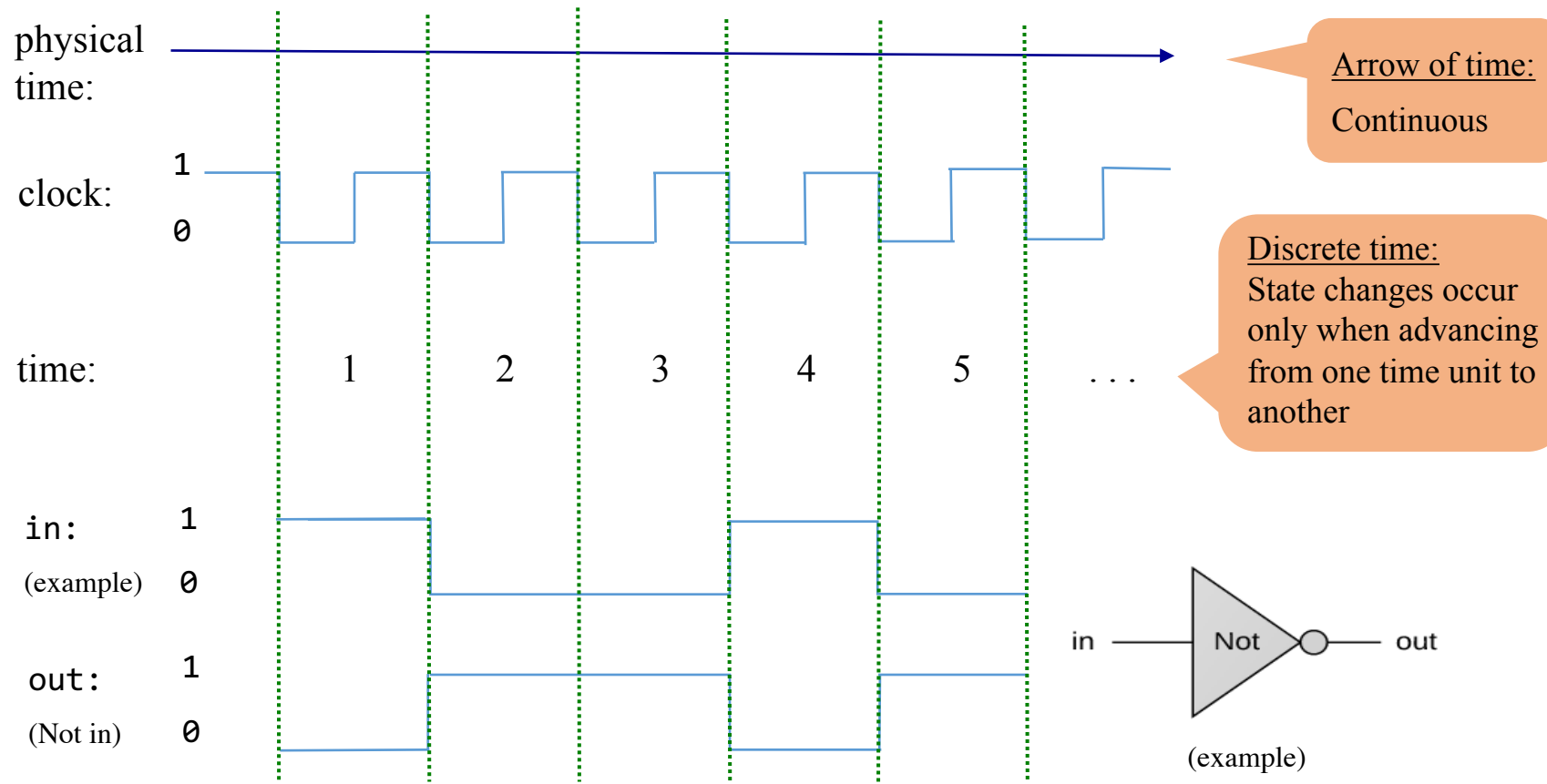


Not: an example of a *combinational chip*:

- The gate reacts “immediately” to the inputs
- Well, not really, but the clock’s behavior creates this effect.

# Combinational logic / sequential logic
 
## Combinational logic:


The output is a pure function of the present input only


 
## Sequential logic:


The output depends on:

- the present input (optionally)
- the history of the input (creates a memory effect).



# Flip-Flop

---


 


The simplest state-keeping gate:

- 1-bit input, 1-bit output
- The gate outputs its previous input:  $out(t) = in(t-1)$
- Implementation: a gate that can flip between two stable states:  
“remembering 0”, or “remembering 1”
- Gates that feature this behavior are called *data flip-flops*.



# Flip-Flop

---

 
 


# Flip-Flop

---

  

# Flip-Flop

  

# DFF implementation notes

---

A DFF bi-state architecture can be built from Nand gates:

- step 1: create an input-output loop,  
achieving a combinational (un-clocked) flip-flop
  - step 2: isolate across time steps using a “master-slave” architecture
- The resulting implementation is elegant, but conceptually confusing

## Technical note

The implementation described above is impossible in our hardware simulator, since:

- The supplied simulator does not permit combinational loops
- A cycle in hardware connections is allowed only if the cycle passes through a sequential (“clocked”) gate

## Implementing sequential chips

- The supplied simulator features a built-in DFF gate
- Sequential chips are implemented by using built-in DFF chip parts.

# Sequential chips

---

Sequential chips are capable of:

- maintaining state, and, optionally,
  - acting on the state, and on the current inputs
- $$\left. \vphantom{\begin{matrix} \bullet \\ \bullet \end{matrix}} \right\} \text{state}(t) = f(\text{state}(t-1), \text{input}(t))$$

Example: DFF

- The DFF state: the value of the input from the previous time unit
- The simplest, most elementary sequential chip

Example: RAM

- The RAM state: the current values of all its registers
- given some address (input), the RAM emits the value of the selected register

Implementation note


- All combinational chips are constructed from Nand gates
- All sequential chips are constructed from DFF gates, and combinational chips.


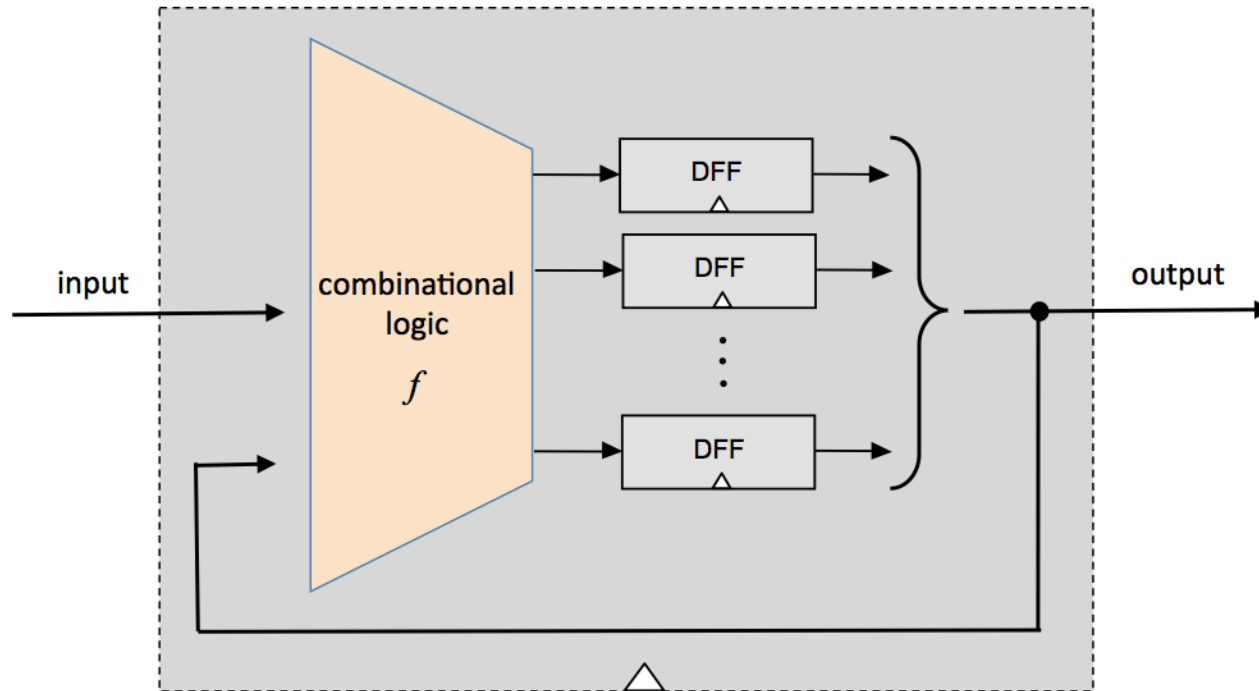
# Sequential chips

---

$$\text{state}(t) = f(\text{state}(t-1), \text{input}(t))$$




## Implementation note

- All combinational chips are constructed from Nand gates
- All sequential chips are constructed from DFF gates, and combinational chips.

# Sequential chip: 1-bit register

---

 


if  $\text{load}(t)$  then  $\text{out}(t+1) = \text{in}(t)$   
else  $\text{out}(t+1) = \text{out}(t)$


- Designed to “remember”, or “store”, a single bit
- More accurately:
  - Stores a bit until...
  - Instructed to load, and store, another bit.

# 1-bit register


---

 

 
if  $\text{load}(t)$  then  $\text{out}(t+1) = \text{in}(t)$   
else  $\text{out}(t+1) = \text{out}(t)$




# 1-bit register

 

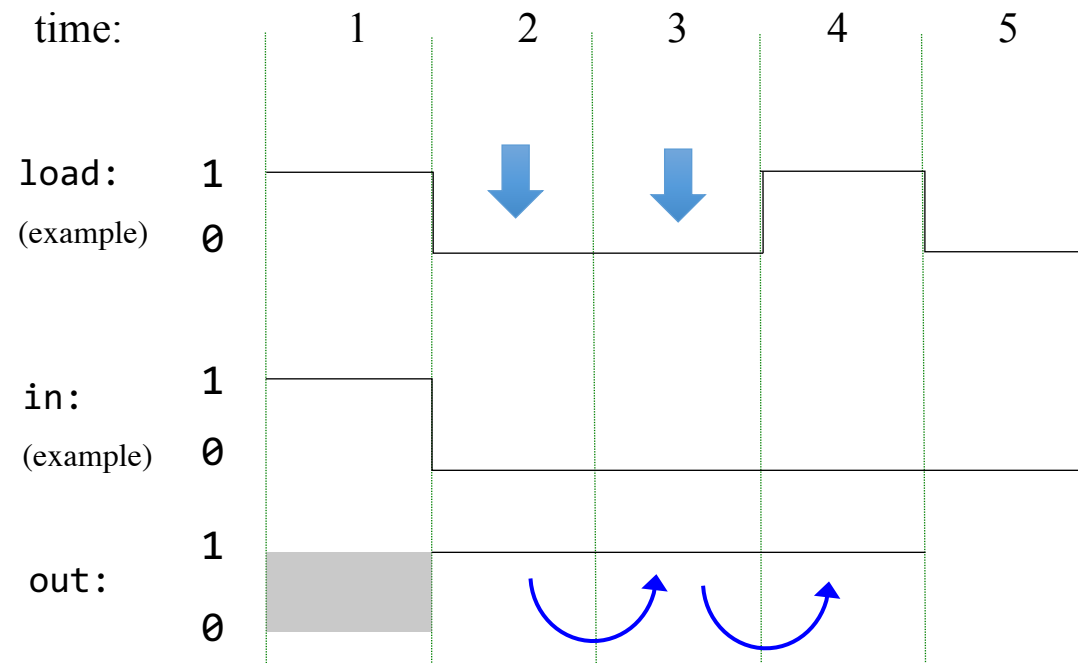
if  $\text{load}(t)$  then  $\text{out}(t+1) = \text{in}(t)$   
else  $\text{out}(t+1) = \text{out}(t)$



# 1-bit register

 

 
if  $\text{load}(t)$  then  $\text{out}(t+1) = \text{in}(t)$   
else  $\text{out}(t+1) = \text{out}(t)$



Resulting behavior:  
Stores and emits a value, until instructed to load (and store) a new value



# 1-bit register implementation – first attempt

---


 


# 1-bit register implementation

---

 
 


# 1-bit register implementation

 
 






# 1-bit register implementation

  



# 1-bit register implementation

  



# 1-bit register implementation

  



## 1-bit register implementation

  

# 1-bit register implementation

 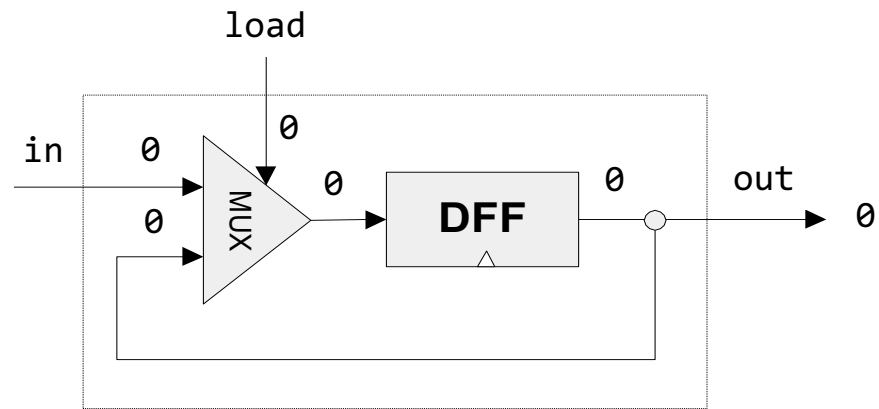

# 1-bit register implementation

 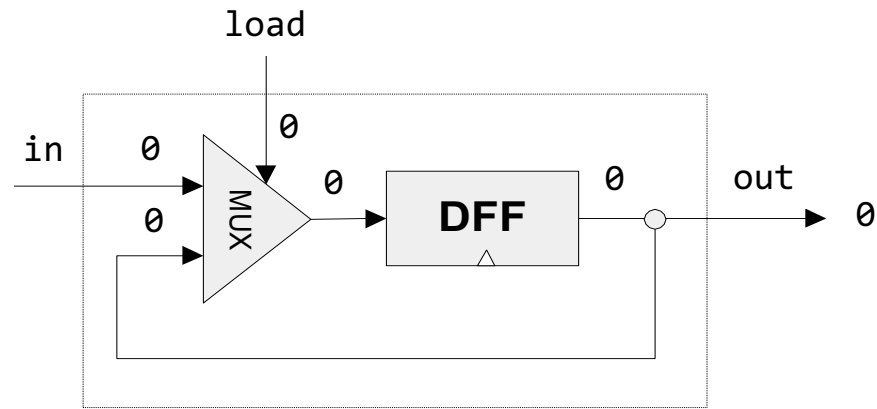

Resulting behavior:  
Stores and emits a value, until instructed to load (and store) a new value

# Chapter 3: Memory

---



Time matters



Sequential logic



Flip Flops



Memory units

- Counters
- Project 3 overview

# Memory units

---

We'll describe (and build) a progression of memory units:



1-bit register:

Designed to store a single bit



Multi-bit register:

Designed to store an  $w$ -bit value (in Hack,  $w = 16$ )


- Random Access Memory (RAM):

Designed to store  $n$  addressable  $w$ -bit values,  
each having a unique *index*, or *address*, ranging from 0 to  $n-1$ .



# Multi-bit register (also known as “register”)

---

 


Word width ( $w$ ):

- 16-bit, 32-bit, 64-bit, ...
- We will focus on 16-bit registers, without loss of generality.

# Register: abstraction

---

 

## To read a Register:

probe out

### Result:

out emits the Register's state

## To set Register = $v$

set in =  $v$


set load = 1

### Result:

- The Register's state becomes  $v$ ;
- From the next cycle onward, out emits  $v$

# Register: implementation

---

 

A  $w$ -bit register can be created from an array of  $w$  1-bit registers.

# Register chip in action

Run the clock

Chip Name: DRegister (Clocked) Time: 0

Input pins		Output pins	
Name	Value	Name	Value
in[16]	17	out[16]	0
load	0		

Set in to 17

Inspect the register's output

Inspect the register's contents

D: 0

For the demo, we use a built-in 16-bit register from the Hack chipset, named Dregister, or simply D.

```
HDL
* This built-in chip implements a 16-bit register
* providing a GUI representation of the register
* called "D register" (typically used in the Hack chip)
*/

CHIP DRegister {
    IN in[16], load;
    OUT out[16];

    BUILTIN DRegister;
    CLOCKED in, load;
}
```

# Register chip in action

Run the clock

Chip Name: DRegister (Clocked) Time: 12

Input pins	
Name	Value
in[16]	17
load	0

Output pins	
Name	Value
out[16]	0

**HDL**

```
* This built-in chip implements a D register,
* providing a GUI representation of the chip.
* called "D register" (typically used in the
*/
CHIP DRegister {
    IN in[16], load;
    OUT out[16];

    BUILTIN DRegister;
    CLOCKED in, load;
}
```

Inspect the register's output

Inspect the register's contents

D: 0

# Register chip in action

Run the clock

Chip Name: DRegister (Clocked) Time: 12+

Input pins		Output pins	
Name	Value	Name	Value
in[16]	17	out[16]	0
load	1		

Set in to 17  
Set load to 1

Inspect the register's output

Inspect the register's contents

D: 17

```
CHIP DRegister {
    IN in[16], load;
    OUT out[16];

    BUILTIN DRegister;
    CLOCKED in, load;
}
```

# Register chip in action

Run the clock

Chip Name: DRegister (Clocked) Time: 13

Input pins		Output pins	
Name	Value	Name	Value
in[16]	17	out[16]	17
load	1		

Inspect the register's output

Inspect the register's contents

```
HDL
/* This built-in chip implements a D register,
 * providing a GUI representation of the register
 * called "D register" (typically used in the
 * CPU).
 */
CHIP DRegister {
    IN in[16], load;
    OUT out[16];

    BUILTIN DRegister;
    CLOCKED in, load;
}
```

D: 17

# Memory units

---

We'll describe (and build) a progression of memory units:



1-bit register:



Multi-bit register:




Random Access Memory (RAM)



# RAM

---

 

## Architecture:

A sequence of  $n$  addressable registers,  
with addresses 0 to  $n-1$


## Address width:

$$k = \log_2 n$$

## Word width:

No impact on the RAM logic  
(Hack computer:  $w = 16$ )

# RAM: abstraction

 

At any given point of time:

- ❑ *one* register in the RAM is selected
- ❑ all the other registers are irrelevant

**To read Register  $i$  :**


set address =  $i$

probe out

**Result:**

out emits the value of Register  $i$

# RAM: abstraction

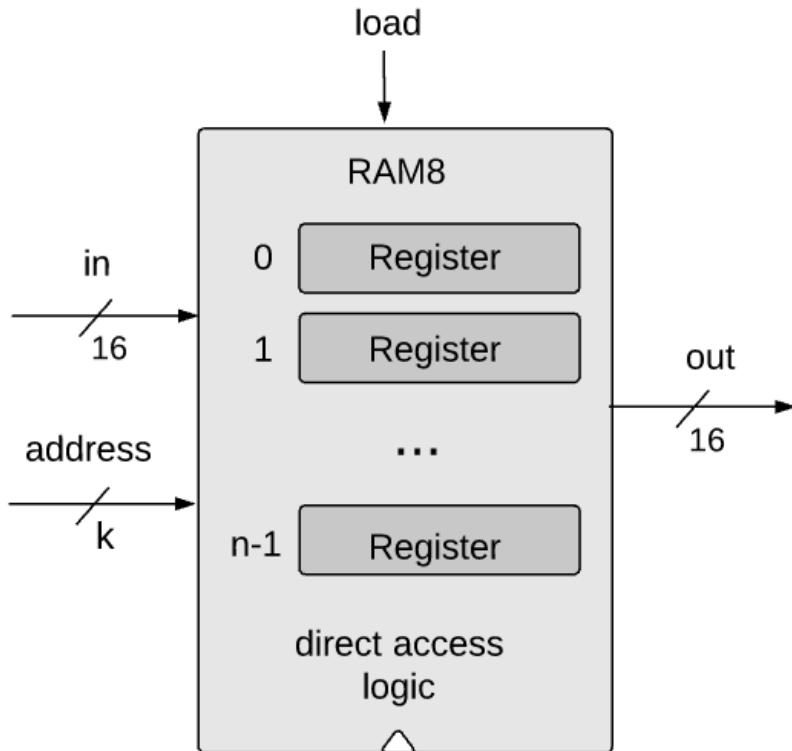

At any given point of time:

- ❑ *one* register in the RAM is selected
- ❑ all the other registers are irrelevant

**To set Register  $i$  to  $v$  :**


set address =  $i$   
set in =  $v$   
set load = 1

**Result:**

- The state of Register  $i$  becomes  $v$
- From the next cycle onward, out emits  $v$

# RAM: abstraction

---

 


## Why “Random Access Memory”?

Irrespective of the RAM size ( $n$ ), every randomly selected register can be accessed “instantaneously”, at more or less the same time.

# A family of 16-bit RAM chips

---

 

chip name	$n$	$k$
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14

Why these particular RAM chips?

Because that's what we need for building the Hack computer.

# RAM chip in action

---



# Chapter 3: Memory

---

 Time matters

 Sequential logic

 Flip Flops

 Memory units

 Counters

- Project 3 overview

# Where counters come to play

---

- The computer must keep track of which instruction should be fetched and executed next
- This control mechanism can be realized by a register called Program Counter
- The PC contains the address of the instruction that will be fetched and executed next
- The PC is designed to support three possible control operations:

Reset: fetch the first instruction

PC = 0

Next: fetch the next instruction

PC++


Goto: fetch instruction  $n$

PC =  $n$



# Program Counter

---

 

```
/**
 * A 16-bit counter with load and reset control bits.
 * if      reset(t) out(t+1) = 0
 * else if load(t)  out(t+1) = in(t)
 * else if inc(t)   out(t+1) = out(t) + 1 (integer addition)
 * else            out(t+1) = out(t)
 */

CHIP PC {
    IN in[16], load, inc, reset;
    OUT out[16];

    PARTS:
    // Put your code here:
}
```

# Counter chip in action

---



# Chapter 3: Memory

---

 Time matters

 Sequential logic

 Flip Flops

 Memory units

 Counters

 Project 3 overview

# Project 3

---

## Given:

- ❑ All the chips built in Projects 1 and 2
- ❑ Flip-Flop (built-in DFF gate)


## Goal: Build the following chips:

- ❑ Bit
- ❑ Register
- ❑ RAM8
- ❑ RAM64
- ❑ RAM512
- ❑ RAM4K
- ❑ RAM16K
- ❑ PC

A family of sequential chips, from  
a 1-bit register to a 16K RAM unit.

# 1-bit register

---

 

Bit.hdl

```
/**
 * 1-bit register:
 * If load(t) then out(t+1) = in(t)
 * else          out(t+1) = out(t)
 */


CHIP Bit {
    IN in, load;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Implementation tip:  
Can be built from a DFF  
and a multiplexor.

# 16-bit Register

---

 

Register.hdl

```
/**
 * 16-bit register:
 * If load(t) then out(t+1) = in(t)
 * else out(t+1) = out(t)
 */


CHIP Register {
    IN in[16], load;
    OUT out[16];

    PARTS:
        // Put your code here:
}
```

Implementation tip:

Can be built from an array  
of sixteen 1-bit registers.

# 8-Register RAM

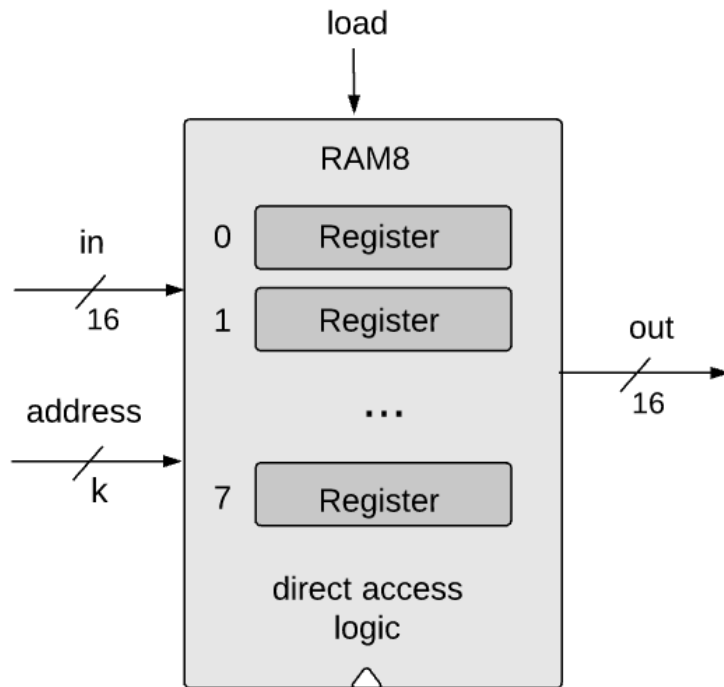

RAM8.hdl

```
/*
 * Let M stand for the state of the
 * register selected by address.
 * if load(t) then {M=in(t), out(t+1)=M}
 * else
 *     out(t+1)=M
 */

CHIP RAM8 {
    IN in[16], load, address[3];
    OUT out[16];

    PARTS:
        // Put your code here:
}
```

## Implementation tips:

- ❑ Feed the in value to all the registers, simultaneously
- ❑ Use mux / demux chips to select the register specified by address.

# Project 3

---

## Given:

- ❑ All the chips built in Projects 1 and 2
- ❑ Flip-Flop (DFF gate)

## Goal: Build the following chips:


- ✓ ❑ Bit
- ✓ ❑ Register
- ✓ ❑ RAM8
  - ❑ RAM64
  - ❑ RAM512
  - ❑ RAM4K
  - ❑ RAM16K
- ❑ PC

} Our next task



# RAM8, RAM64, ... RAM16K

---

 

Same technique  
can be used to  
implement RAM4K  
and RAM16K

## Implementation tips

- A RAM unit can be built by grouping smaller RAM-parts together
- Think about the RAM's address input as consisting of two fields:
  - one field can be used to select a RAM-part;
  - the other field can be used to select a register within that RAM-part
- Use mux/demux logic to effect this addressing scheme.

# Project 3

---


## Given:

- ❑ All the chips built in Projects 1 and 2
- ❑ Flip-Flop (DFF gate)

## Goal: Build the following chips:

- ✓ ❑ Bit
- ✓ ❑ Register
- ✓ ❑ RAM8
- ✓ ❑ RAM64
- ✓ ❑ RAM512
- ✓ ❑ RAM4K
- ✓ ❑ RAM16K
- ❑ PC

# Program Counter

 

## Implementation tip:

Can be built from a register, an incrementor, and some logic gates.

```
/**
 * A 16-bit counter with load, inc, and reset control bits.
 *
 * if reset(t)    out(t+1)=0           // resetting: counter = 0
 * else if load(t) out(t+1)=in(t)       // setting counter = value
 * else if inc(t)  out(t+1)=out(t)+1    // incrementing: counter++
 * else           out(t+1)=out(t)       // counter does not change
 */

CHIP PC {
    IN in[16], load, inc, reset;
    OUT out[16];

    PARTS:
        // Implementation comes here.
}
```

# Project 3 resources

From NAND to Tetris  
Building a Modern Computer From First Principles  
www.nand2tetris.org

Home

Prerequisites

Syllabus

Course

Book

Software

Terms

Papers

Talks

Cool Stuff

About

Team

Q&A

Project 3: Sequential Chips

Background

The computer's main memory, also called *Random Access Memory*, or *RAM*, is an addressable sequence of  $n$ -bit registers, each designed to hold an  $n$ -bit value. In this project you will gradually build a RAM unit. This involves two main issues: (i) how to use gate logic to store bits persistently, over time, and (ii) how to use gate logic to locate ("address") the memory register on which we wish to operate.

Objective

Build all the chips described in Chapter 3 (see list below), leading up to a *Random Access Memory* (RAM) unit. The only building blocks that you can use are primitive DFF gates, chips that you will build on top of them, and chips described in previous chapters.

Chips

Chip (HDL)	Description	Test script	Compare file
DFF	Data Flip-Flop (primitive)		
Bit	1-bit register	Bit.tst	Bit.cmp
Register	16-bit register	Register.tst	Register.cmp
RAM8	16-bit / 8-register memory	RAM8.tst	RAM8.cmp
RAM64	16-bit / 64-register memory	RAM64.tst	RAM64.cmp
RAM512	16-bit / 512-register memory	RAM512.tst	RAM512.cmp
RAM4K	16-bit / 4096-register memory	RAM4K.tst	RAM4K.cmp
RAM16K	16-bit / 16384-register memory	RAM16K.tst	RAM16K.cmp
PC	16-bit program counter	PC.tst	PC.cmp

All the necessary project 3 files are available in:  
nand2tetris / projects / 03

Nand to Tetris / www.nand2tetris.org / Chapter 3 / Copyright © Noam Nisan and Shimon Schocken

Slide 60

## More resources

---

- HDL Survival Guide
- Hardware Simulator Tutorial
- nand2tetris Q&A forum



All available in: [www.nand2tetris.org](http://www.nand2tetris.org)

# Best practice advice

---

- Try to implement the chips in the given order
- If you don't implement some of the chips required in project 3, you can still use them as chip-parts in other chips. Just rename the given stub-files; this will cause the simulator to use the built-in versions of these chips
- You can invent new, “helper chips”; however, this is not required: you can build any chip using previously-built chips only
- Strive to use as few chip-parts as possible.
- You will have to use chips from Projects 1 and 2
- Best practice: use their built-in versions
- For technical reasons, the HDL files of this project are organized in two directories named `a` and `b`
- This directory structure should remain as is.

# Chapter 3: Memory

---

- ✓ Time matters
- ✓ Sequential logic
- ✓ Flip Flops
- ✓ Memory units
- ✓ Counters
- ✓ Project 3 overview



## Chapter 3

# Memory

These slides support chapter 3 of the book

*The Elements of Computing Systems*

By Noam Nisan and Shimon Schocken

MIT Press